

# 上海交通大学试卷

( 2023~2024-1 Academic Year/Fall Semester )

Class No. \_\_\_\_\_ Name in English or Pinyin: \_\_\_\_\_

Student ID No. \_\_\_\_\_ Name in Hanzi(if applicable): \_\_\_\_\_

## ECE2150J/VE215 Introduction to Circuits

### Final Exam

**2023/December/12th 10:00 – 11:40 am**

The exam paper has 15 pages in total.

**You are to abide by the University of Michigan-Shanghai Jiao Tong University Joint Institute (UM-SJTU JI) honor code. Please sign below to signify that you have kept the honor code pledge.**

#### THE UM-SJTU JI HONOR CODE

**I accept the letter and spirit of the honor code:**

**I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code by myself or others.**

**Signature:** \_\_\_\_\_

**Please enter grades here:**

<b>Exercises No.</b> <b>题号</b>	<b>Points</b> <b>得分</b>	<b>Grader's Signature</b> <b>流水批阅人签名</b>
1		
2		
3		
4		
5		
<b>Total 总分</b>		

## Q1. Discrete small questions. (20 points)

Please note that letters in **bold** indicate a **phasor form** of elements/parameters.

Q1.1 If  $v_1 = 30 \sin(\omega t + 10^\circ)$  and  $v_2 = 20 \sin(\omega t + 50^\circ)$ , which of these statements are true? (3 Points)

(a)  $v_1$  leads  $v_2$


(b)  $v_2$  leads  $v_1$

(c)  $v_2$  lags  $v_1$

(d)  $v_1$  lags  $v_2$

(e)  $v_1$  and  $v_2$  are in phase

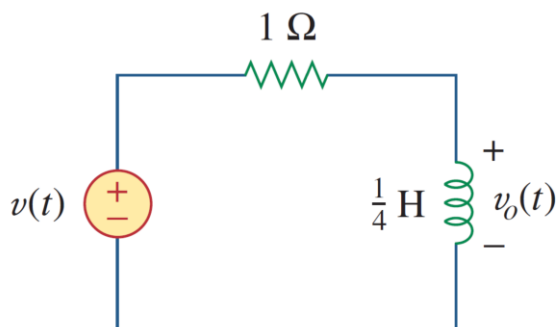Q1.2 At what frequency will the output voltage  $v_o(t)$  in the figure below be equal to the input voltage  $v(t)$ ? (3 points)



(a) 0 rad/s

(b) 1 rad/s

(c) 4 rad/s

(d)  $\infty$  rad/s

(e) None of the above

Q1.3 A source is connected to three loads  $\mathbf{Z}_1$ ,  $\mathbf{Z}_2$ , and  $\mathbf{Z}_3$  in parallel. Which of these is not true? (4 points)

(a)  $\mathbf{P} = \mathbf{P}_1 + \mathbf{P}_2 + \mathbf{P}_3$

(b)  $\mathbf{Q} = \mathbf{Q}_1 + \mathbf{Q}_2 + \mathbf{Q}_3$

(c)  $\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \mathbf{S}_3$

(d)  $\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \mathbf{S}_3$

(e) None of the above

Q1.4 Which of these is not a required condition for a balanced system? (4 points)

(a)  $|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$


(b)  $\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$

(c)  $\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$

(d) Source voltages are  $120^\circ$  out of phase with each other.

(e) Load impedances for the three phases are equal.

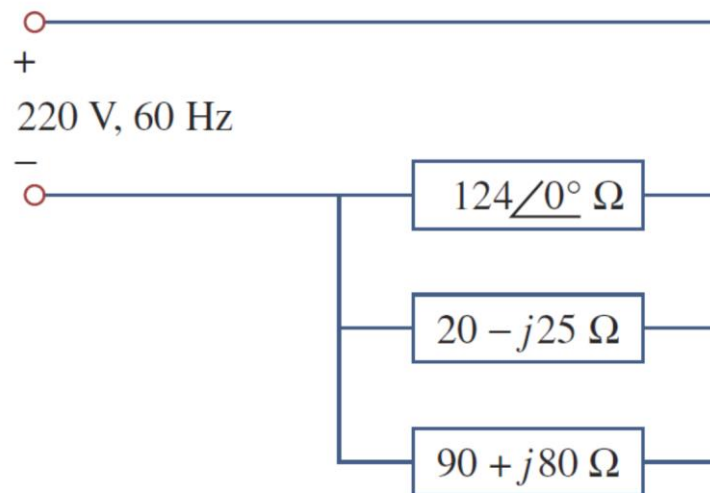Q1.5 For the power system below, find the average power, the reactive power, and the power factor. Note that 220 V is the **rms value**. (6 points)




Q2. A residential wiring circuit is shown below. In this model, the resistor  $R_3$  is used to model a 250 V appliance, and the resistors  $R_1$  and  $R_2$  are used to model 125 V appliances. The branches carrying  $I_1$  and  $I_2$  are modeling what electricians refer to as the hot conductors in the circuit, and the branch carrying  $I_3$  is modeling the neutral conductor. (18 points)

(a) Show that  $I_n$  is zero if  $R_1 = R_2$ . (6 points)


(b) Show that  $V_1 = V_2$  if  $R_1 = R_2$ . (3 points)

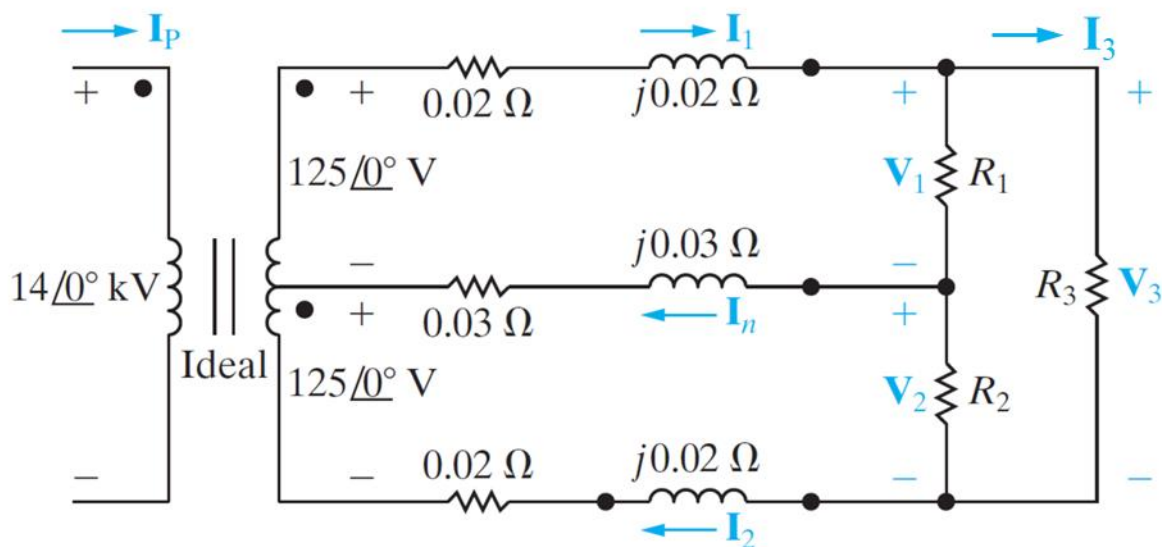(c) If  $R_1 = 40 \Omega$ ,  $R_2 = 400 \Omega$ , and  $R_3 = 8 \Omega$ , please compare  $V_1$  and  $V_2$  with and without the neutral line. And please explain the need of the neutral line. *Hint*: The circuit with the neutral line has  $I_1 = 34.2 - j0.18$  A and  $I_2 = 31.4 - j0.16$  A. (9 points)




(c) An open neutral can result in severely unbalanced voltages across the 125 V loads at  $R_1$  and  $R_2$ . (+2)

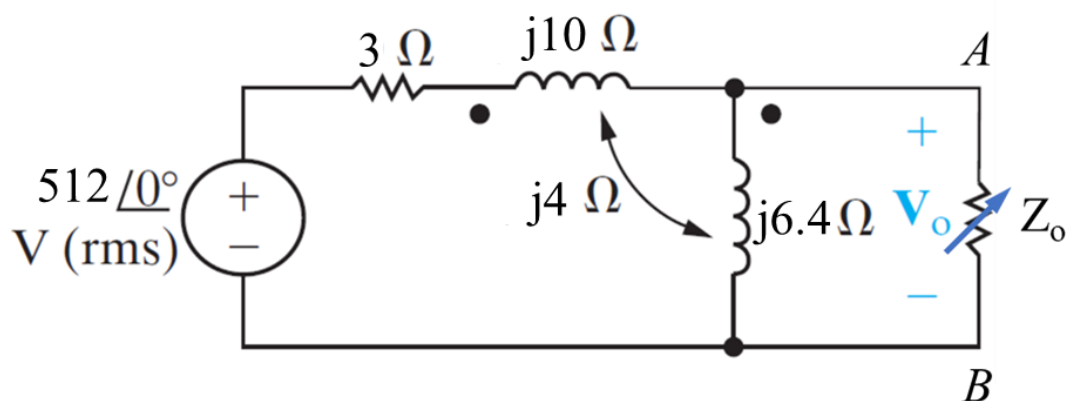Q3. Assume a variable impedance  $Z_o$  is adjusted for maximum average power transfer to  $Z_o$ . Please answer the following questions. (18 points)



(a) Please draw the equivalent circuit using the dependent voltage sources as the example below shows. (4 points)

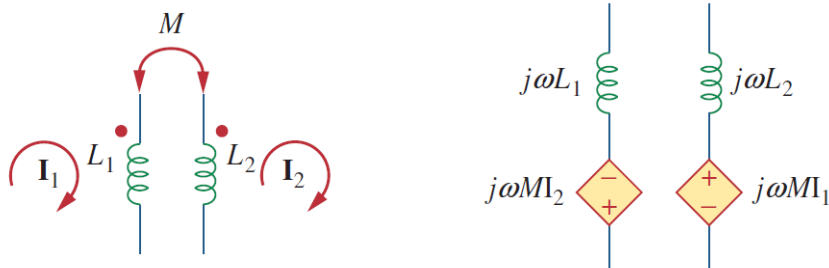*Example:* Magnetically coupled circuit and its equivalent circuit with dependent voltage sources.




(b) Find open circuit voltage  $V_{OC} = V_{TH}$ , and short circuit current  $I_{SC} = I_N$  at the terminal between  $A$  and  $B$ . (8 points)

(c) Find the equivalent impedance at the terminal between  $A$  and  $B$ . (2 points)

(d) What is the maximum average power that can be delivered to  $Z_o$ ? (4 points)

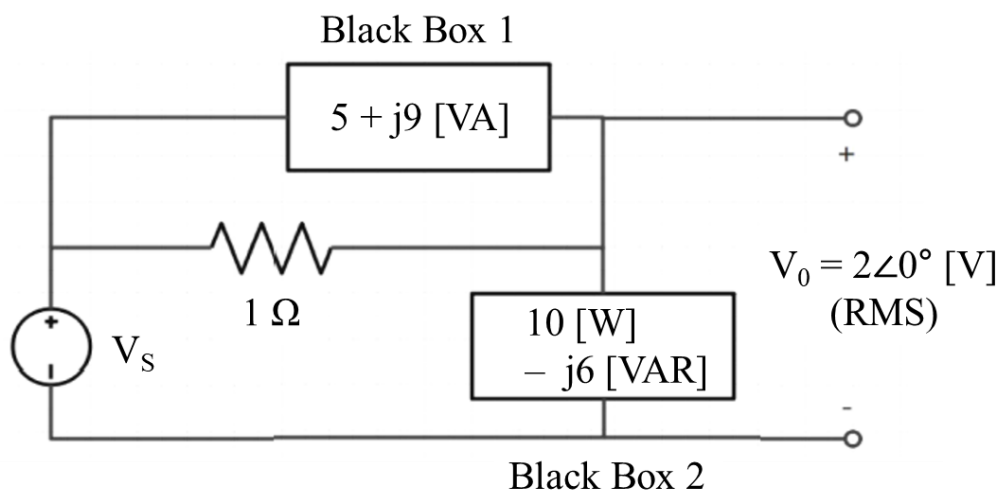Q4. In the circuit below, the two black boxes are composed of linear, passive circuit elements (resistors, capacitors, and inductors) without a power source. (24 points)




- (a) Please draw the power triangles of the two black boxes and then determine its type, i.e. leading or lagging. (4 points)
- (b) Please find all possible values of source voltage  $V_s$ . Please use a phasor form. **Hint:** Current through resistor is a complex number. (12 points)
- (c) Suppose the angular frequency of the source is  $100\ \text{rad/s}$  and you want to correct the overall power factor by connecting pure reactive loads in parallel with the source. Please calculate all possible values of such additional capacitance (or inductance) that will change the overall power factor to  $0.95$  for all possible  $V_s$ . (8 points)



Q5. The circuit below shows a balanced source, a-b-c sequence three phase system. Line impedance ( $Z_l$ ) is  $Z$ , load impedance ( $Z_L$ )  $\Delta$  and Y is  $Z$ , respectively, and source impedance ( $Z_s$ ) is  $Z_s$ . Suppose  $V_{an}$  is  $V_S \angle \theta$ . Both  $\Delta$  and Y load impedances are present.

(20 points)

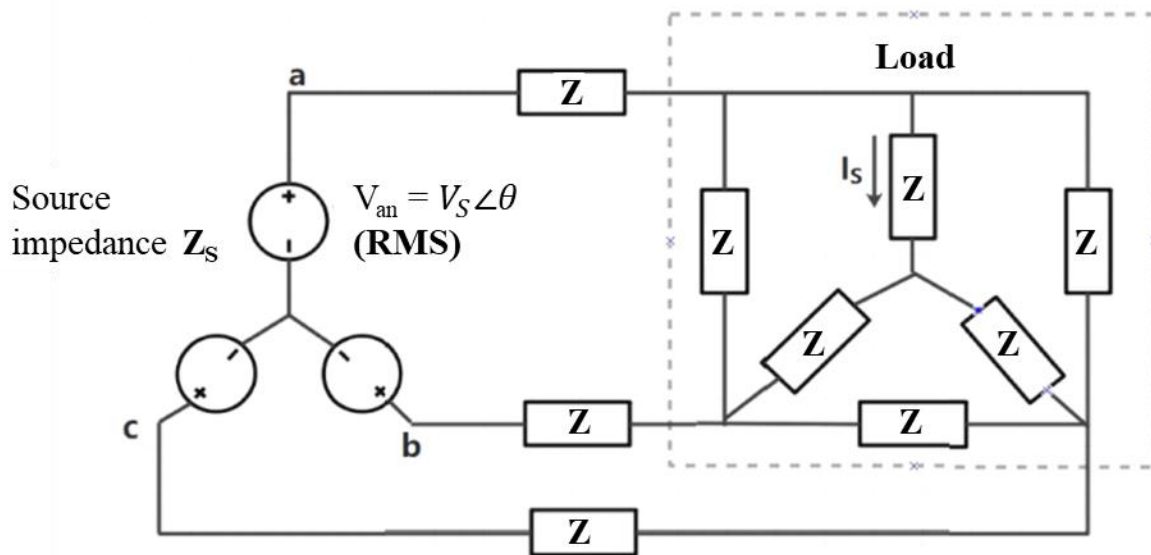

- Find an equivalent circuit in the Y-Y form. Please mark values of  $Z_s$ ,  $Z_l$ , and  $Z_L$  clearly. (4 points)
- Derive line currents and the voltage drops caused by the line ( $Z_l$ ) and load impedance ( $Z_L$ ) of three lines. (6 points)
- Please derive the total complex power absorbed by the loads ( $Z_L$ ). (6 points)
- Please derive  $I_s$ . (4 points)


Q1.5

220 Vrms, 60Hz

$$S_1 = \frac{220^2}{124 \angle 0^\circ} = 390.22$$

$$S_2 = \frac{220^2}{20 + j25} = 944.4 - j1180.5$$
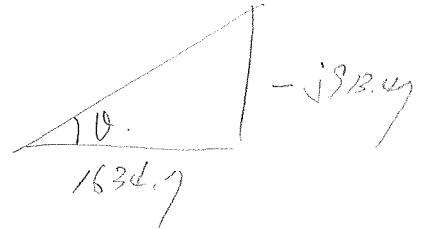
$$S_3 = \frac{220^2}{90 - j80} = 300 + j267.03$$



$$P = 390.22 + 944.4 + 300 = 1634.7 \text{ [W]} \text{ (+2)}$$

$$Q = -j1180.5 + j267.03 = -j913.47 \text{ or } 913.47 \text{ leading [VAR]} \text{ (+2) (+1)}$$

$$pf = 0.8732 \text{ (+1)}$$

finding total complex power is okay

but needs to specify leading or lagging  
otherwise -1

Q2.

(a)  $I_1$  loop.

$$(0.02 + j0.02)I_1 + R(I_1 - I_3) + (0.03 + j0.03)(I_1 - I_2) = 125 \quad (1) \quad (+1)$$

$I_2$  loop.

$$(0.02 + j0.02)I_2 + (0.03 + j0.03)(I_2 - I_1) + R(I_2 - I_3) = 125 \quad (2) \quad (+1)$$

$$(1) - (2) \Rightarrow (0.08 + j0.08 + R)I_1 - (0.08 + j0.08 + R)I_2 = 0.$$


$$\text{or } (0.08 + j0.08 + R)I_1 = (0.08 + j0.08 + R)I_2 \quad (+2)$$

$$\underline{I_1 = I_2} \quad \text{thus, } \underline{I_n = 0} \quad \text{Proof } (+2)$$

$$(b) \quad V_1 = R_1(I_1 - I_3) \quad V_2 = R_2(I_2 - I_3) \quad (+1)$$

$$\text{if } R_1 = R_2 \Rightarrow \underline{I_1 = I_2} \quad (+1) \quad \text{thus, } \underline{V_1 = V_2} \quad (+1)$$

(c) (i) without neutral line.

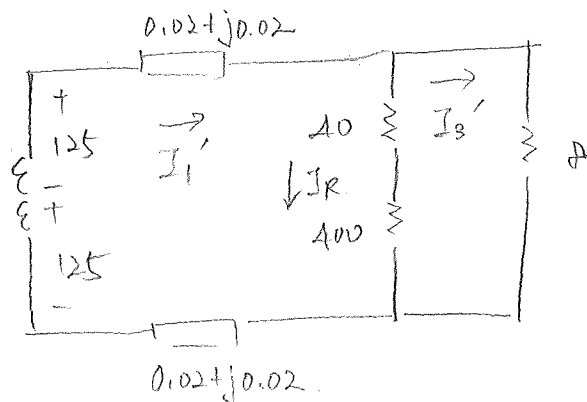

for (a) and (b)

other methods are okay  
as long as they are right  
with clear processes  
or logic.

$$① (0.04 + j0.04)I_1' + 440(I_1' - I_2') = 250.$$

$$② 440(I_2' - I_1') + 8I_3' = 0.$$

Solve the above.  $I_1' = 31.66 - j0.16 \text{ (+1)}$

$$I_3' = 31.09 - j0.16 \text{ (+1)}$$

$$I_R = I_1' - I_3' = \underline{0.57}.$$

$$V_1 = 40 \times 0.57 = \underline{22.8} \text{ (+1)}$$

$$V_2 = 400 \times 0.57 = \underline{228} \text{ (+1)}$$

(ii) with neutral line.

we get ①  $(40.05 + j0.05)I_1 - (0.03 + j0.03)I_2 - 40I_3 = 125$

$$② -(0.03 + j0.03)I_1 + (400.05 + j0.05)I_2 - 400I_3 = 125$$


$$③ -40I_1 - 400I_2 + 448I_3 = 0$$

Since  $I_1 = 34.19 - j0.18$  and  $I_2 = 31.4 - j0.16$ .

$$\underline{I_3 = 31.09 - j0.16 \text{ (+1)}}$$


$$V_1 = 40(I_1 - I_3) = 124.2 \angle -0.35^\circ \text{ (+1)}$$
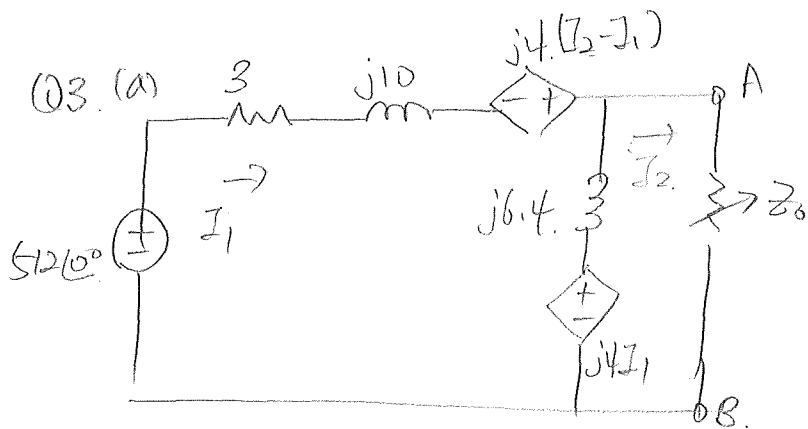
$$V_2 = 400(I_2 - I_3) = 124.4 \angle -0.18^\circ \text{ (+1)}$$



by setting the current  $I_1$  and  $I_2$  direction as above  
mutual voltage  $< 0$


(b)  $I_{OC} \Rightarrow I_2 = 0$ .

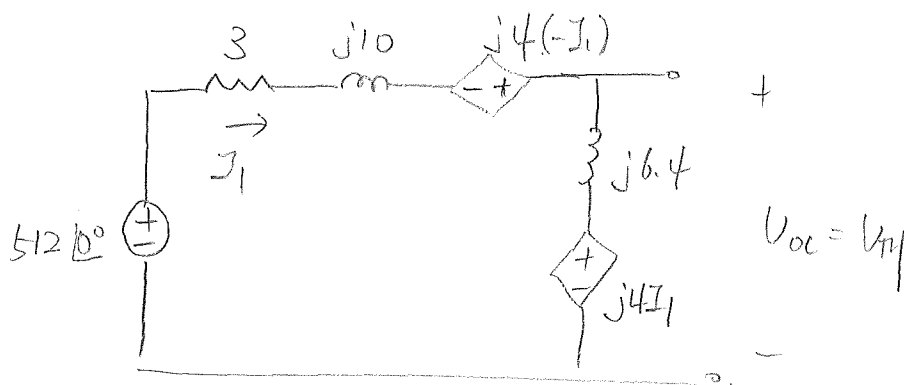

$$-512 + (3 + j10)I_1 + j4I_1 + j6.4I_1 + j4I_1 = 0 \quad (+1)$$

$$I_1 = \frac{512}{3 + j24.4} = \frac{2.57 - j20.66}{20.83 \angle -82.90^\circ} \quad (+1)$$
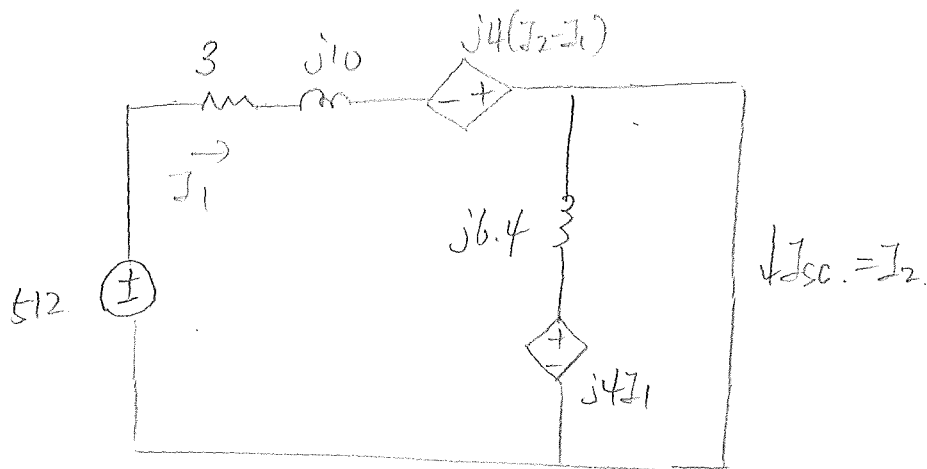
$$V_{TH} = j6.4 \times I_1 + j4 \times I_1 = \frac{216.53 \angle 7.1^\circ}{(+1)} \quad (+1)$$



$$\textcircled{1} \quad -512 + (3+j10)I_1 - j4(I_2 - I_1) + j6.4(I_1 - I_2) + j4I_1 = 0 \quad (+1)$$


$$\textcircled{2} \quad -j4I_1 + j6.4(I_2 - I_1) = 0 \quad (+1)$$

$$\text{Solving } \textcircled{1} \text{ and } \textcircled{2} \quad \underline{I_{sc} = I_2 = 301.25 - j95.63} \quad (+2)$$

$$= 102.99 \angle -68.20^\circ$$

$$(c) \underline{Z_{Th} = \frac{V_{oc}}{I_{sc}} = 2.10 \angle 15.3^\circ} \quad (+2)$$

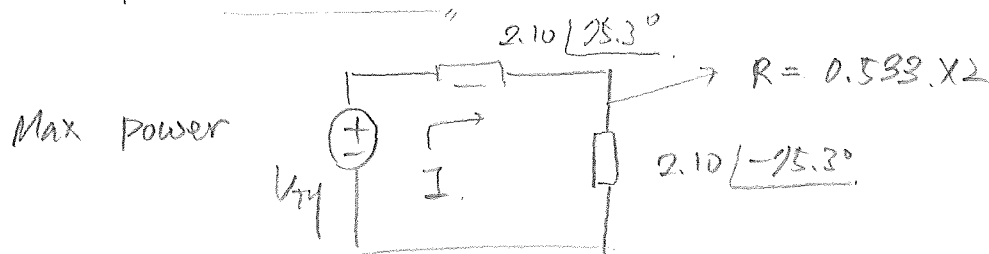
$$(d) \underline{Z_0 = Z_{Th}^* = 2.10 \angle -15.3^\circ} \quad (+2)$$




$$\underline{I = \frac{216.53 \angle 0.1^\circ}{0.583 \times 2} = 203.12 \angle 2.1^\circ} \quad (+1)$$

$$\underline{P_{max} = 203.12^2 \times 1.583 = 21.99 \text{ kW}} \quad (+2)$$

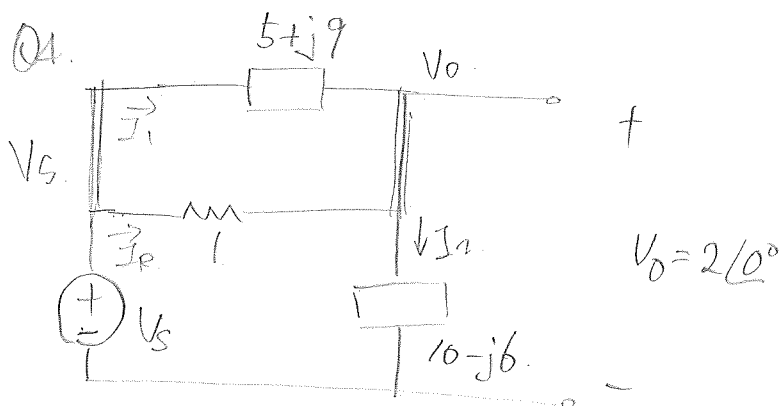$\frac{V_{Th}}{2R_{Th}}$  is based on Peak Value not RMS.




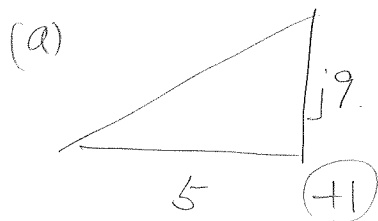→ with or without  $j$   
either is okay.



$$pf = \cos \tan^{-1} \frac{9}{5} = 0.49$$

Lagging. (+1)

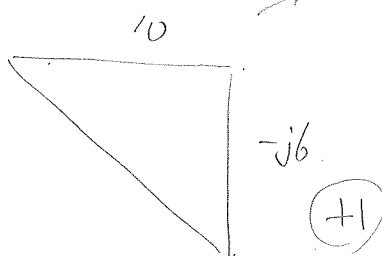

$$pf = \cos \tan^{-1} \frac{-6}{10} = 0.86$$

Leading. (+1)

(b) Black box 2.

$$S_2 = V_o \times I_2^* = 10-j6 \Rightarrow I_2^* = \frac{10-j6}{2\angle 0^\circ} = 5-j3$$

thus  $I_2 = 5+j3$  (+2)

Voltage at R,  $V_R = V_s - V_o = I_R \times 1$

$I_R = V_s - 2$  or  $a+jb$ . (+1)

by KCL  $I_2 = I_1 + I_R$ ,  $I_1 = (5-a) + j(3-b)$  (+1)

Black box 1

$$S_1 = (V_s - 2) I_1^* = (a+jb) \times (5-a + j(3-b)) = 5+j9$$

$$P = 5a - a^2 + 3b - b^2 = 5$$
 (+1)

$$Q = -3a + 5b = 9$$
 (+1)

Solve P and Q we get  $a = 0.8$  and  $b = 2.28$  (+1)

or  $a = 2.61$  and  $b = 3.37$  (+1)

therefore, by  $V_s - 2 = a + jb$ .

$$V_s = 2.8 + j2.28 \text{ or } 3.61 \angle 39.16^\circ \quad (+2)$$

$$\text{or } V_s = 4.61 + j3.37 \text{ or } 5.71 \angle 36.17^\circ \quad (+2)$$


(C)  $\omega = 100 \text{ rad/s}$

Q) for  $V_s = 3.61 \angle 39.16^\circ$  or  $2.8 + j2.28$

$$\begin{aligned} \text{At } R, S_R &= (2.8 + j2.28 - 2)(0.8 - j2.28) \\ &= 0.8^2 + 2.28^2 = \underline{5.84} \end{aligned}$$

$$\text{total } S = 5 + j9 + 10 - j6 + 5.84 = 20.84 + j3$$
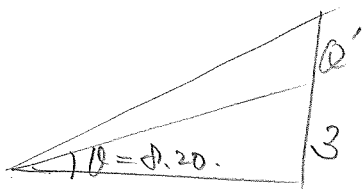
$$PF = 0.9898 \quad \theta = 8.20^\circ \quad (+1)$$



PF to be 0.95  $\theta = 18.19^\circ$

inductor needed. (+1)

$$\tan \theta' = \frac{Q' + 3}{20.84}$$

$$Q' = 3.85 \text{ VAR}$$

$$3.85 = \frac{3.61^2}{100 \times L}$$

$$L = 0.034 \text{ H.} \quad (+2)$$




② for  $V_s = 5.71 \angle 36.1^\circ$  or  $4.61 + j3.37$

$$S_R = (4.61 + j3.37 - 2) (2.61 - j3.37) = 2.61^2 + 3.37^2 = 18.17$$

total  $S = 5 + j9 + 10 - j6 + 18.17 = 33.17 + j3 \Rightarrow PF = 0.9859$  (+1)

$\theta = 5.71^\circ$

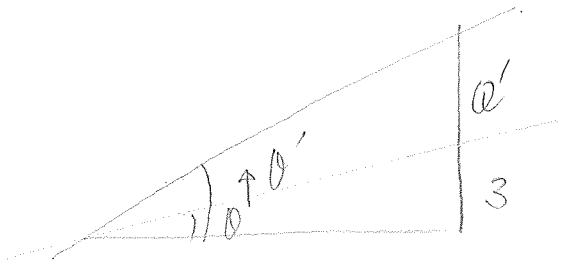


PF to be 0.95  $\theta' = 18.19$  inductor is needed. (+1)

$$\tan \theta' = \frac{Q' + 3}{33.17} \quad Q' = 7.90 \text{ VAR required.}$$

$$7.90 = \frac{5.71^2}{100 \times L} \quad \underline{L = 0.044 \text{ H}} \quad (+2)$$

Q5. (a) change  $\gamma$  load to  $\Delta$ .



$$Z_{\Delta} = 3Z_{\gamma}$$

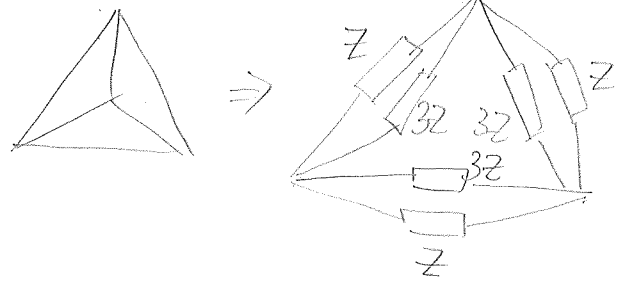

Now we have two parallel  $\Delta$  with the values of  $Z$  and  $3Z$ .

$$Z_{\Delta-\text{eq}} = \frac{3Z^2}{3Z+Z} = \frac{3}{4}Z \quad (+1)$$

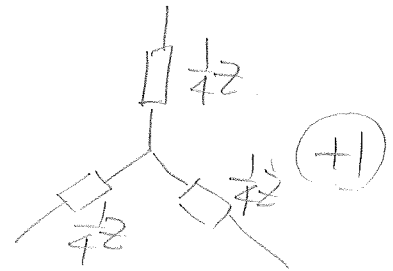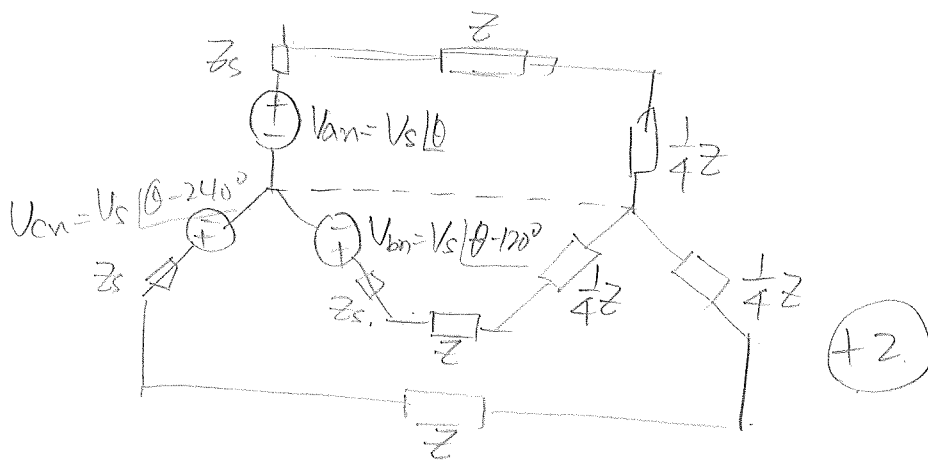Change  $\Delta$  back to  $\gamma$ ,  $Z_{\gamma} = \frac{1}{3}Z_{\Delta}$



(b)  $\gamma$ - $\gamma$  circuit. Line current = phase current.

$$I_a = \frac{V_s \angle 0^\circ}{Z_s + Z + \frac{1}{3}Z} = \frac{V_s \angle 0^\circ}{Z_s + \frac{4}{3}Z}$$

$$I_b = \frac{V_s \angle 0^\circ - 120^\circ}{Z_s + \frac{4}{3}Z}, \quad I_c = \frac{V_s \angle 0^\circ - 240^\circ}{Z_s + \frac{4}{3}Z} \quad \text{each } (+1)$$

Line voltage drop by  $Z_L$  and  $Z_L$ .  
 // define as  $V_L$ .

$$V_{L-a} = \frac{V_s \angle 0}{Z_s + \frac{5}{4}Z} \times \left( Z + \frac{1}{4}Z \right) = \frac{\frac{5}{4}Z \times V_s \angle 0}{Z_s + \frac{5}{4}Z} \quad \text{each } (+1)$$

$$V_{L-b} = \frac{\frac{5}{4}Z \times V_s \angle 0 - 120^\circ}{Z_s + \frac{5}{4}Z}, \quad V_{L-c} = \frac{\frac{5}{4}Z \times V_s \angle 0 - 240^\circ}{Z_s + \frac{5}{4}Z}$$


typo it shows (b)

$$(C) \quad S_a = I_a^2 Z_Y = \frac{1}{4}Z \times \frac{V_s^2}{(Z_s + \frac{5}{4}Z)^2} \quad (+3)$$

thus total complex power  $S = 3 \times S_a = \frac{3}{4}Z \times \frac{V_s^2}{(Z_s + \frac{5}{4}Z)^2} \quad (+3)$

typo it shows (c).

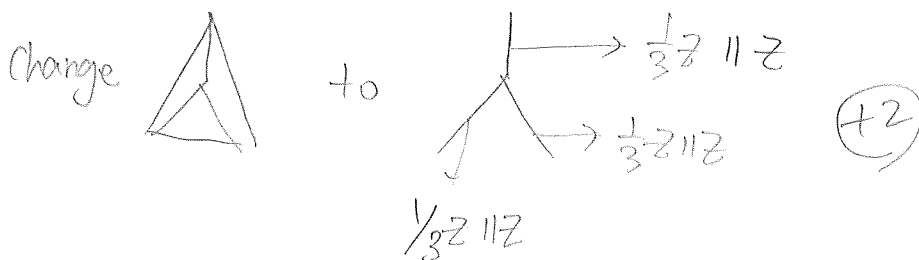(d) in Y-Y, we have  $I_a = \frac{V_s \angle 0}{Z_s + \frac{5}{4}Z}$



by current division,  $I_s = \frac{\frac{1}{3}Z}{\frac{1}{3}Z + Z} \frac{V_s \angle 0}{Z_s + \frac{5}{4}Z}$

$$= \frac{1}{4} \frac{V_s \angle 0}{Z_s + \frac{5}{4}Z} \quad (+2)$$